

## Lab #6 - Oscilloscope/Logic Analyzer

Isai Mercado Oliveros

Oct 15, 2014

### Toggle circuit Verilog code

```
//  
/////////////////////////////////////  
module Toogle(GCLK, CLR, Qout, Clk_out);  
    input GCLK, CLR;  
    output Qout, Clk_out;  
    wire n;  
  
    //FF_DC(q, clk, clr, d); input clk, clr, d; output reg q;  
    FF_DC hi (Qout,GCLK,CLR,n);  
    not(n,Qout);  
    buf(Clk_out,GCLK);  
  
endmodule
```


### Toggle circuit screen capture



### Toggle circuit question and answer (Why is wave not square?)

Because Analogous signals are never a square


### Bounce circuit screen capture

 

### Bounce circuit settling time

440 us


#### 4-bit Shifter screen capture

 

#### 4-bit Shifter pattern of values

0,4,D,1,2,A,B,6,8,7,9,F,E,C,3,5,0
 
### 16-bit Shifter screen capture (start at 4290 Hex)



### 16-bit Shifter four values (start at 4290 Hex)

4290,8521,1A43, 34A6, 694C



16-bit Shifter screen capture (990ns after triggered pattern)



16-bit Shifter value (990ns after triggered pattern)

0B6B

### 16-bit Shifter screen capture (16.38us after triggered pattern)



### 16-bit Shifter value (16.38us after triggered pattern)

4290

### 16-bit Shifter total number of values in repeating pattern

819

### Anomalies (bugs, problems, and suggestions)

The lab is hard because using the oscilloscope is hard, but other than that it is pretty straight forward.