

Lab #5 - Arithmetic Logic Unit – ALU

Isai Eliseo Mercado Oliveros

Oct 8, 2014

Procedure

Full Adder and 4:1 Mux Verilog codes

```
//  
////////////////////////////////////  
module FullAdder (A,B,Cin,Cout,Sum) ;  
    input A,B,Cin;  
    output Cout,Sum;  
    wire c0,c1,c2;  
  
    xor (Sum, A,B,Cin) ;  
    and (c0,A,B) ;  
    and (c1,A,Cin) ;  
    and (c2,B,Cin) ;  
    or (Cout,c0,c1,c2) ;  
  
endmodule
```

```
//  
////////////////////////////////////  
module Mux4to1 (Out,A,B,C,D,Sel1,Sel2) ;  
    input A,B,C,D,Sel1,Sel2;  
    output Out;  
  
    assign Out = (Sel1 == 0 && Sel2 == 0) ? A :  
                |(Sel1 == 0 && Sel2 == 1) ? B :  
                (Sel1 == 1 && Sel2 == 0) ? C :  
                (Sel1 == 1 && Sel2 == 1) ? D : Out;  
  
endmodule
```

Full Adder and 4:1 Mux TCL files

```
FullAdder.tcl - Notepad
File Edit Format View Help
|#add all signals to the waveform viewer
wave add / -radix hex

#define how the data input signals will behave when you run the simulation
#the command "isim force add (signal) 0 -time 0 -value 1 -time 20ns -repeat 40ns" means that (signal)
#will have a value of 0 from time 0, then change to 1 at time 20ns, and then repeat that cycle every 40ns
isim force add B 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add A 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add cin 0 -time 0 -value 1 -time 40ns -repeat 80ns

#Nothing will change in the waveform viewer until you run the simulation for some period of time.
run 80ns
```

```
Mux4to1.tcl - Notepad
File Edit Format View Help
|#add all signals to the waveform viewer
wave add / -radix hex

#define how the data input signals will behave when you run the simulation
#the command "isim force add (signal) 0 -time 0 -value 1 -time 20ns -repeat 40ns" means that (signal)
#will have a value of 0 from time 0, then change to 1 at time 20ns, and then repeat that cycle every 40ns
isim force add sel1 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add sel2 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add A 0 -time 0 -value 1 -time 40ns -repeat 80ns
isim force add B 0 -time 0 -value 1 -time 80ns -repeat 160ns
isim force add C 0 -time 0 -value 1 -time 40ns -repeat 320ns
isim force add D 0 -time 0 -value 1 -time 80ns -repeat 640ns


#Nothing will change in the waveform viewer until you run the simulation for some period of time.
run 640ns
```

Full Adder and 4:1 Mux simulation waveforms

Adder



Mux

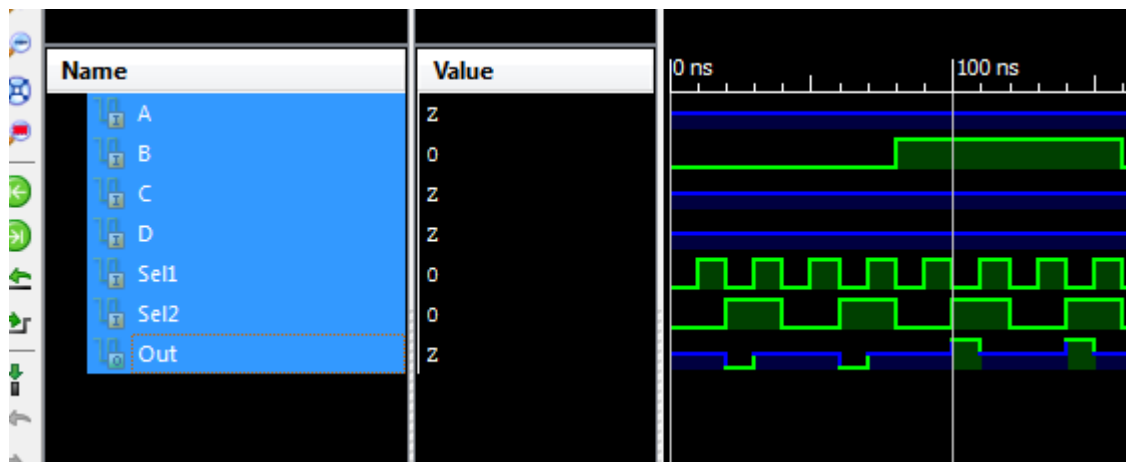

1 bit ALU Verilog code

```
20 //////////////////////////////////////////////////
21 module ALU1bit(Result,Cout,A,B,Cin,Sel1,Sel2);
22     input  A,B,Cin,Sel1,Sel2;
23     output Result,Cout;
24     wire  Sum,Aout,AandB,notA,CarryOut;
25
26     CarryControl CC(Sel1,Sel2,CarryOut,Cout); //module CarryControl(Sel1,Sel2,Cin,Cout);
27     FullAdder FA(A,B,Cin,CarryOut,Sum); //module FullAdder(A,B,Cin,Cout,Sum);
28     OtherLogic OL(Aout,AandB,notA,A,B); //module OtherLogic(Aout,AandB,notA,A,B);
29     Mux4to1 FO(Result,Aout,Sum,AandB,notA,Sel1,Sel2); //module Mux4to1(Out,A,B,C,D,Sel1,Sel2);
30 endmodule
31 |
```


1 bit ALU TCL file

```
ALU1bit.tcl - Notepad
File Edit Format View Help
#add all signals to the waveform viewer
wave add / -radix hex

#define how the data input signals will behave when you run the simulation
#the command "isim force add (signal) 0 -time 0 -value 1 -time 20ns -repeat 40ns" means that (signal)
#will have a value of 0 from time 0, then change to 1 at time 20ns, and then repeat that cycle every 40ns
isim force add A 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add B 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add cin 0 -time 0 -value 1 -time 40ns -repeat 80ns
isim force add Sel1 0 -time 0 -value 1 -time 80ns -repeat 160ns
isim force add Sel2 0 -time 0 -value 1 -time 160ns -repeat 320ns

#Nothing will change in the waveform viewer until you run the simulation for some period of time.
run 320ns
```


1 bit ALU simulation waveform

 

4 bit ALU Verilog code

```
19 //
20 ///////////////////////////////////////////////////////////////////
21 module ALU4bits (A,B,Cin,Cout,Result, Sel1, Sel2);
22     input [3:0] A;
23     input [3:0] B;
24     input Cin, Sel1, Sel2;
25     output Cout;
26     output [3:0] Result;
27     wire [2:0] C;
28     ALU1bit a1 (Result[0], C[0], A[0], B[0], Cin, Sel1, Sel2); //module ALU1bit (Result,Cout,A,B,Cin, Sel1, Sel2);
29     ALU1bit a2 (Result[1], C[1], A[1], B[1], C[0], Sel1, Sel2);
30     ALU1bit a3 (Result[2], C[2], A[2], B[2], C[1], Sel1, Sel2);
31     ALU1bit a4 (Result[3], Cout, A[3], B[3], C[2], Sel1, Sel2);
32 endmodule
33
```

4 bit ALU TCL file

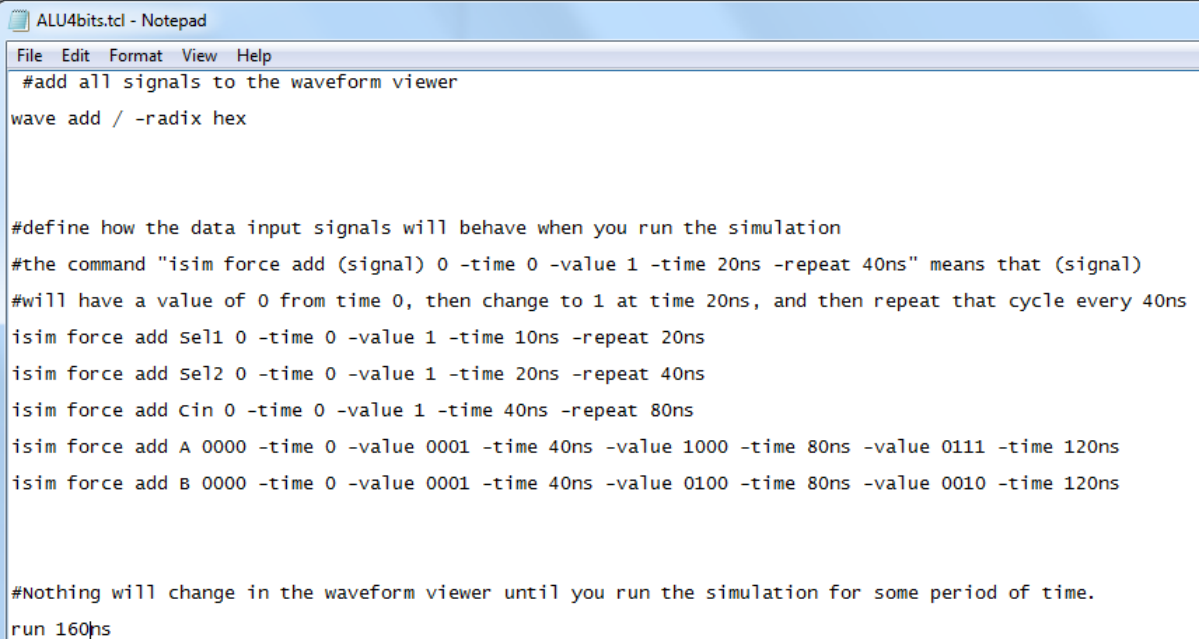


```
ALU4bits.tcl - Notepad
File Edit Format View Help
#add all signals to the waveform viewer
wave add / -radix hex

#define how the data input signals will behave when you run the simulation
#the command "isim force add (signal) 0 -time 0 -value 1 -time 20ns -repeat 40ns" means that (signal)
#will have a value of 0 from time 0, then change to 1 at time 20ns, and then repeat that cycle every 40ns
isim force add Sel1 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add Sel2 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add Cin 0 -time 0 -value 1 -time 40ns -repeat 80ns
isim force add A 0000 -time 0 -value 0001 -time 40ns -value 1000 -time 80ns -value 0111 -time 120ns
isim force add B 0000 -time 0 -value 0001 -time 40ns -value 0100 -time 80ns -value 0010 -time 120ns

#Nothing will change in the waveform viewer until you run the simulation for some period of time.
run 160ns
```

4 bit ALU simulation waveform

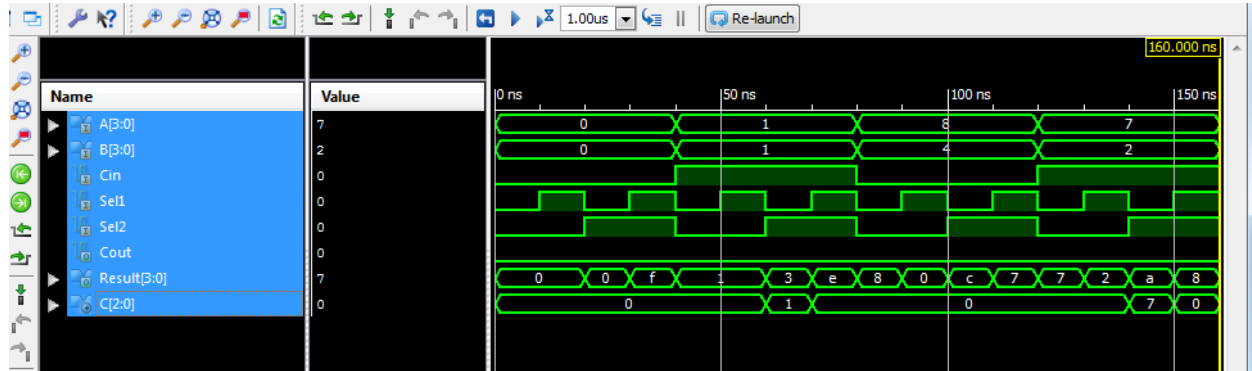

4 bit ALU UCF file

Anomalies (bugs, problems, and suggestion)

I did not have problems and the TAs were really helpful.